

---

## EZRADIOPRO<sup>®</sup> LAYOUT DESIGN GUIDE

---

### 1. Introduction

The purpose of this application note is to help users design EZRadioPRO<sup>®</sup> PCBs using design practices that allow for good RF performance. This application note also help designers by separating TX and RX concerns.

The RF performance and the critical maximum peak voltage on the output pin strongly depend on the PCB layout as well as the design of the matching networks. For optimal performance, Silicon Labs recommends the use of the PCB layout design hints described in the following sections.

### 2. Design Recommendations when Using EZRadioPRO RF ICs

- Extensive testing has been completed using reference designs provided by Silicon Labs. It is recommended to designers to use the reference designs “as-is” since they minimize detuning effects caused by parasitics, component placement, and PCB routing.
- When layouts cannot be followed as shown by the reference designs (due to PCB size and shape limitations), the following layout design rules are recommended.

#### 2.1. Guidelines for Layout Design when Using the Si4430/31


The Si4430/31 devices use a Class-E type TX matching network with a typical output power level of +13 dBm at VDD = 3.3 V. Two basic types of board layout configurations exist at all frequency bands: the Split TX/RX type and the Direct Tie type. In the Split TX/RX type, the TX and RX paths are separated, and individual SMA connectors are provided for each path. In the Direct Tie type, the TX and RX paths are connected together directly, without any additional RF switch. The operating principle of both types and the reference designs with element values are given in “AN436: Si4030/4031/4430/4431 PA Matching” for wirewound and multilayer type 0402 size SMD inductances as well.

The Split and Direct Tie type boards have slightly different PCB layouts, which are described in separate sections.

##### 2.1.1. Split Type Matching Network Layout Based upon the 4431-T-B1\_B Test Card (Separate TX and RX Paths with Two Antennas)


Examples shown in this section of the guide are based upon the layout of the 4431-T-B1\_B test cards. These cards contain two separate antennas for the TX and RX paths. This type of test card is best suited for demonstrating the output power and sensitivity of the EZRadioPRO RFICs. For this purpose, the TX and RX path layouts are separated and isolated as much as possible to minimize the mutual coupling effects. This type of test card is recommended for laboratory evaluation and not for range tests because the presence of two closely-spaced antennas may cause “shadowing” when receiving a radiated signal.

The main layout design concepts are reviewed through this layout to demonstrate the basic principles. However, for an actual application, the layouts of the test cards with a single antenna (or with antenna diversity) should be used as references. The schematic of the Split type matching network for Si4431 RevB1 is shown in Figure 1.

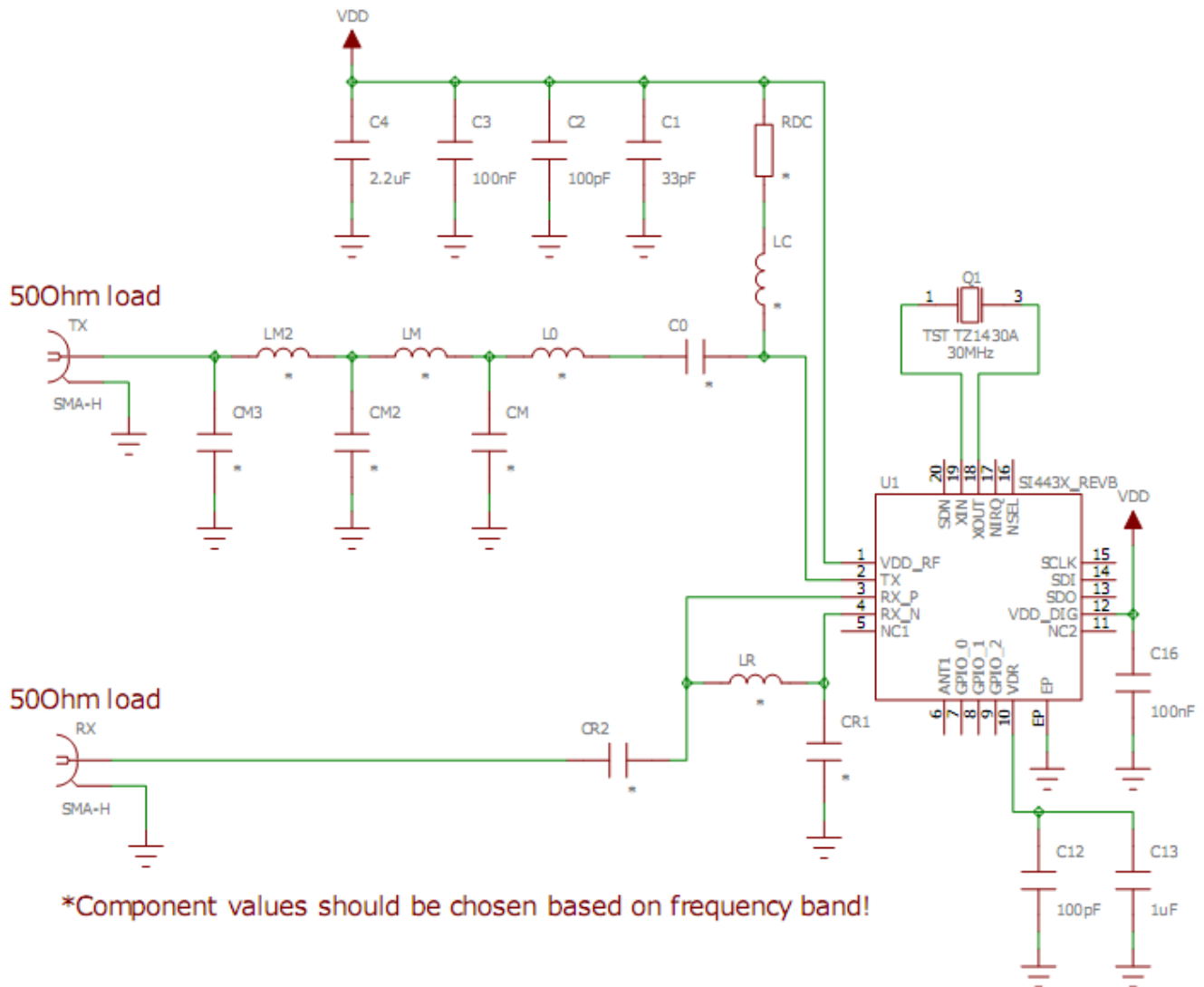

**Figure 1. Schematic of the Split Type Matching Network for the Si4431 RevB1**

The layout structure of the Split type matching network is shown in Figure 2.

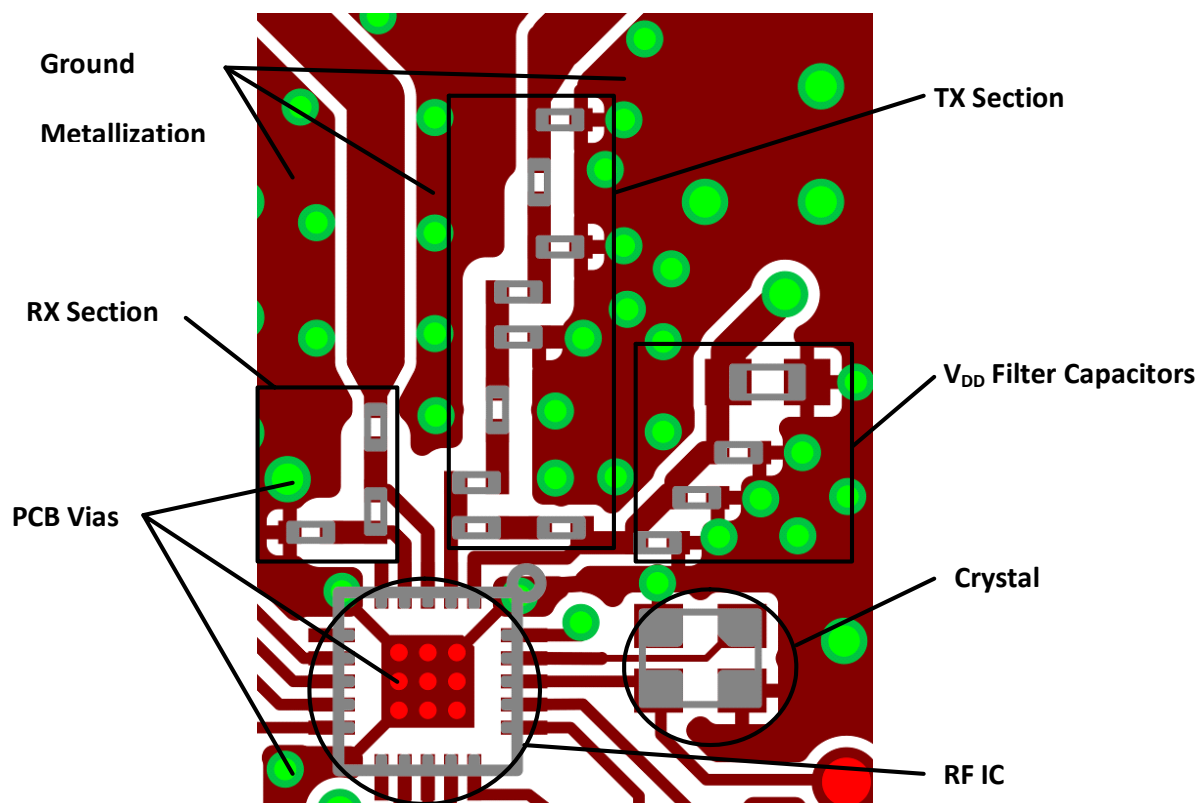


**Figure 2. Split Type Matching Network Layout Structure**

### 2.1.2. Layout Design Guidelines

- The choke inductor (LC) should be placed as close to the TX pin of the RF IC as possible (even if this means the RX is further away).
- The parallel inductor in the RX path (LR) should be perpendicular to the choke inductor (LC) in the TX path because this will reduce TX-to-RX coupling.
- The TX and RX sections should be separated by a GND metal on the top layer to reduce coupling.
- The neighboring matching network components should be placed as close to each other as possible in order to minimize any PCB parasitic capacitance to ground and the series parasitic inductances between the components.
- Increase the grounding effect in the thermal straps used with capacitors. In addition, thicken the trace near the GND pin of these capacitors. This will minimize series parasitic inductance between the ground pour and the GND pins. Additional vias placed close to the GND pin of capacitors (thus connecting it to the bottom layer GND plane) will further help reduce these effects.


Figure 3 illustrates the positioning and orientation of the LC and LR components, the separating GND metal between the TX and RX sections, and thermal strapping on the shunt capacitors.

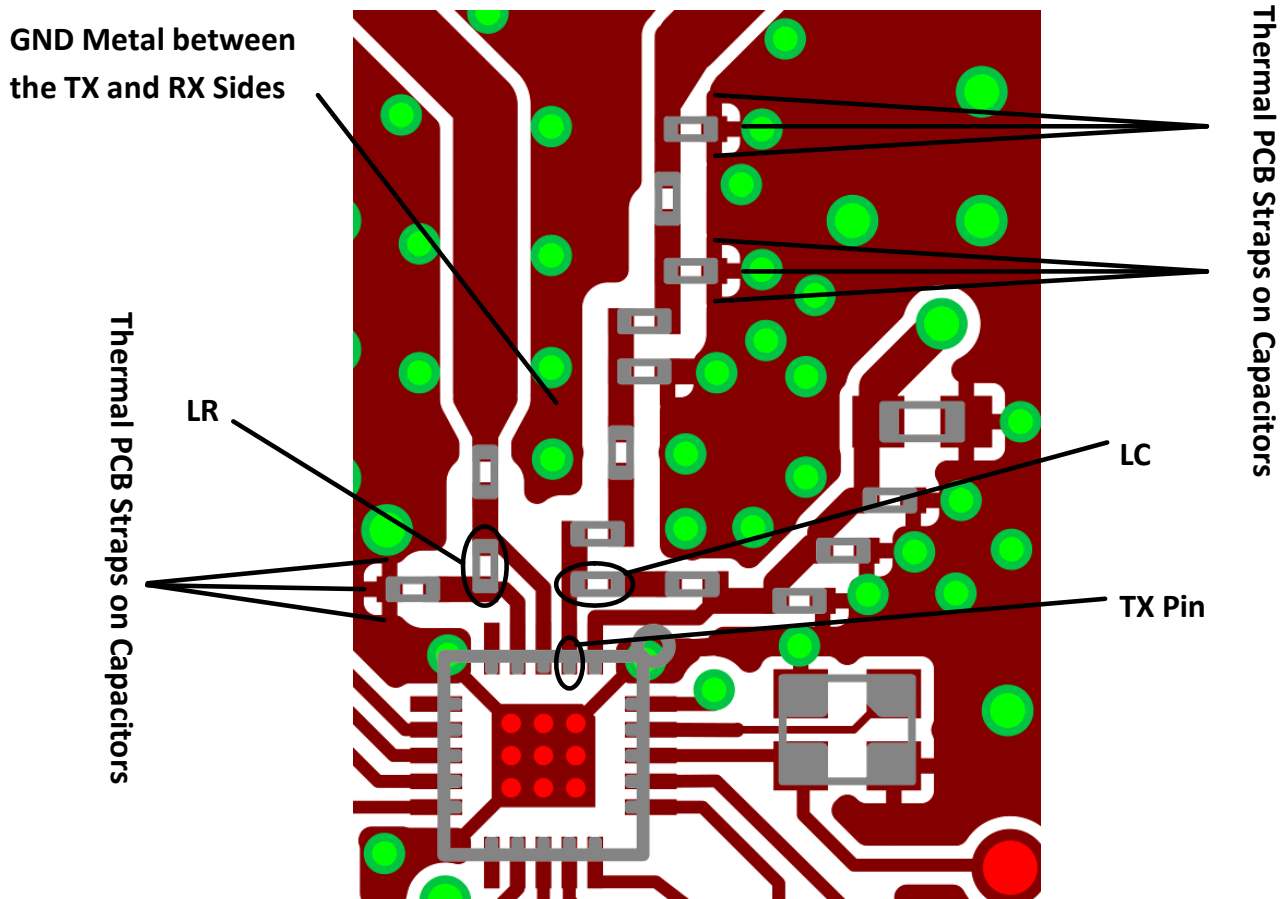

**Figure 3. Si4331 Component Orientation, Placement, and GND Metallization**

- Nearby inductors of the TX path should be kept perpendicular to each other to reduce coupling between stages of the low-pass filter and match. This helps to improve filter attenuation at higher harmonic frequencies.
- Use at least 0.5 mm separation between traces/pads to the adjacent GND pour in the areas of the matching networks. This minimizes the parasitic capacitance and reduces detuning effects.


Figure 4 illustrates the orientation of the inductors of the TX path and the separation of the matching network traces/pads from the GND metal.

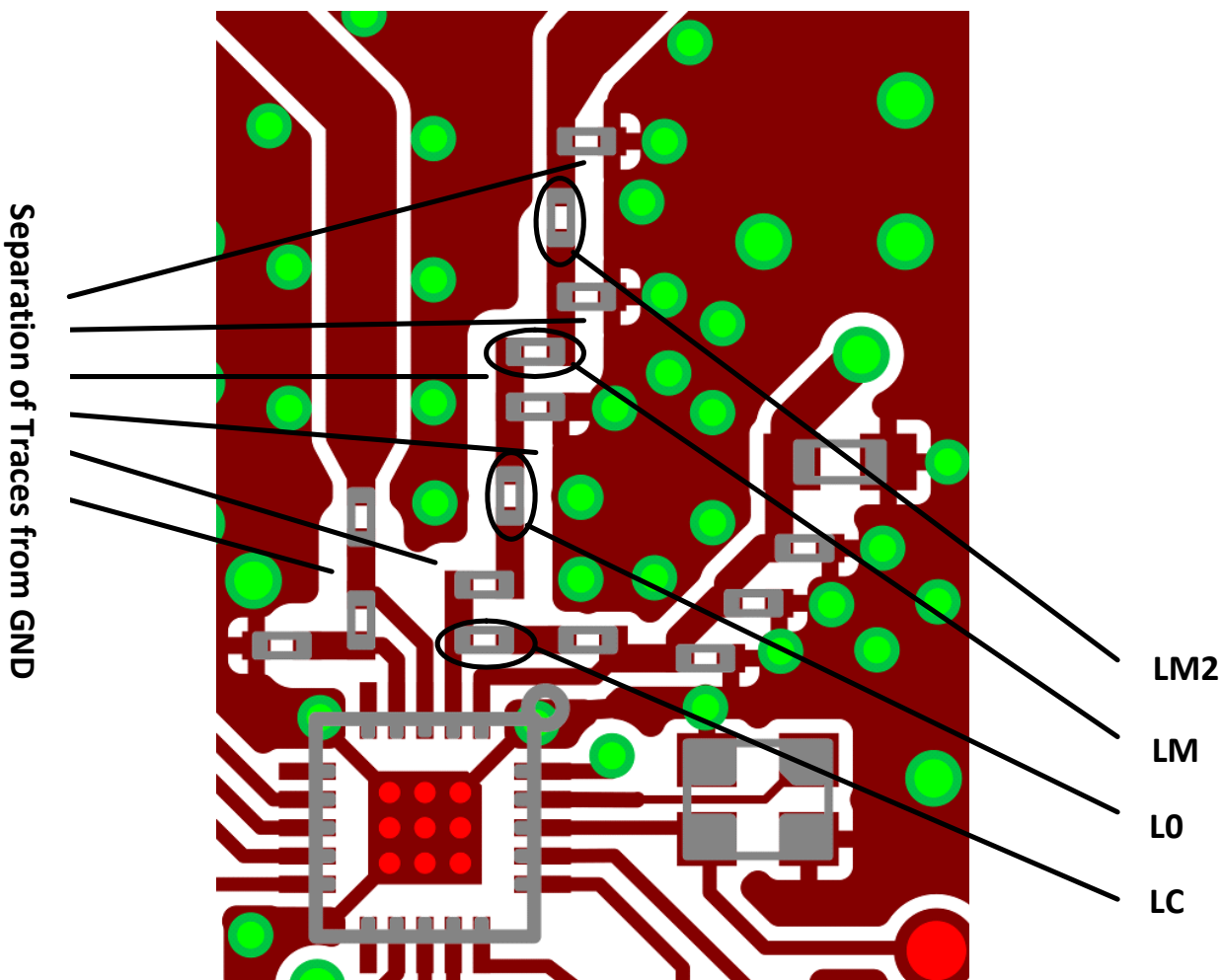

**Figure 4. TX Side Inductor Orientation, Thermal Strapping, and Separation from GND**

- The smaller VDD bypass capacitors ( $C1 = 33 \text{ pF}$  and  $C2 = 100 \text{ pF}$ ) should be kept as close to the VDD pin as possible.
- The exposed pad footprint for the paddle of the RF IC should use as many vias as possible to ensure good grounding and heatsink capability. In the reference designs, there are nine vias, each with 12 mil diameter. The paddle ground should also be connected to the top layer GND metal (if possible) to further improve RF grounding; this may be accomplished with diagonal trace connections through the corners of the RFIC footprint.
- The crystal should be placed as close as possible to the RFIC to ensure that wire parasitic capacitances are kept as low as possible; this reduces any frequency offsets that may occur.
- Place ground metal between the crystal and the VDD trace to reduce coupling effects.

Figure 5 illustrates the grounding of the RFIC, the crystal, and VDD filter capacitor positions, and the isolating ground metal between the VDD trace and the crystal.

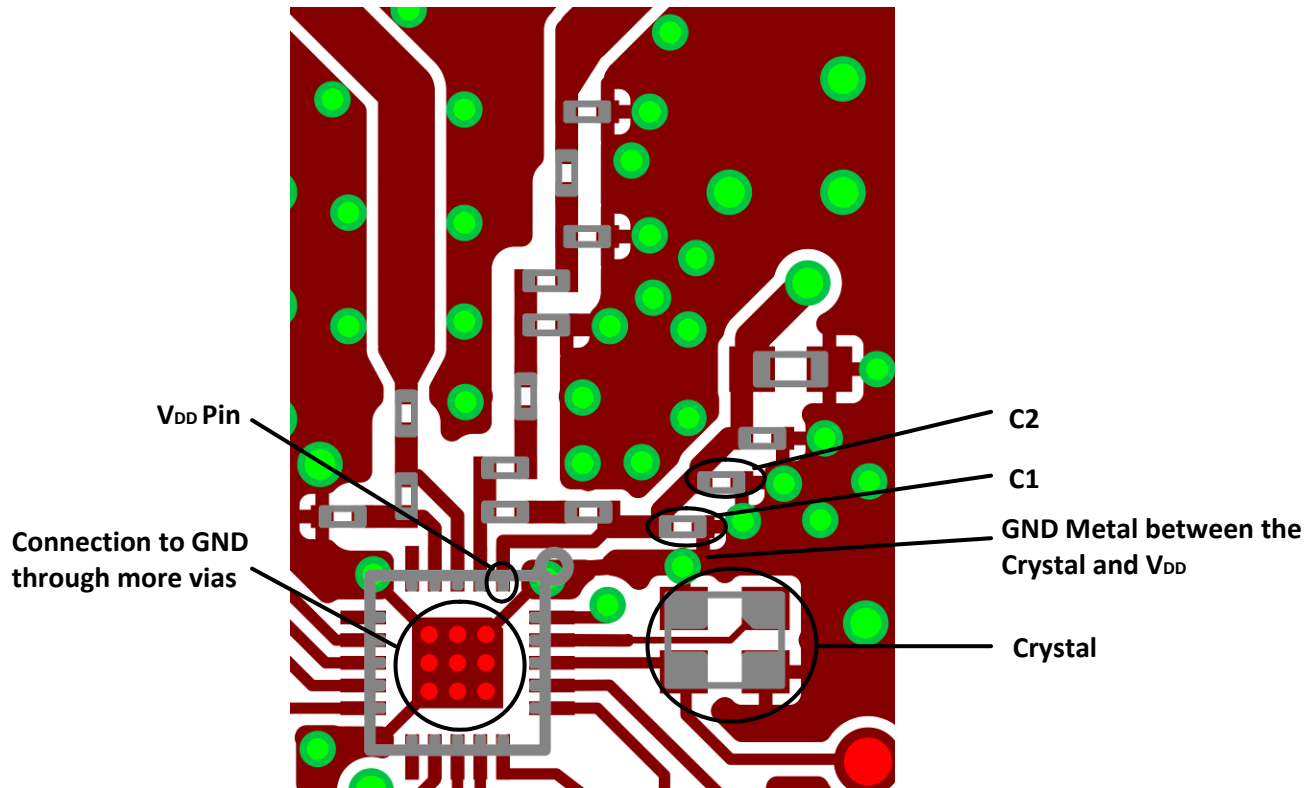

**Figure 5. RFIC GND Vias and GND Metallization**

- To achieve good RF ground on the layout, it is recommended to add large, continuous GND metallization on the top layer in the area of the RF section (at a minimum). Better performance may be obtained if this is applied to the entire PCB. To provide a good RF ground, the RF voltage potentials should be equal along the entire GND area because this helps maintain good VDD filtering and provides a good ground plane for a monopole antenna. Ideally, gaps should be filled with GND metal, and the resulting sections on the top and bottom layers should be connected with as many vias as possible.
- The area under the matching network (on the bottom layer) should be filled with ground metal because this helps reduce or eliminate radiation emissions. Board routing and wiring should not be placed in this region to prevent coupling effects with the matching network. It is also recommended that the GND return path between the GND vias of the TX LPF/Match and the GND vias of the RFIC paddle should not be blocked in any way; the return currents should see a clear unhindered pathway through the GND plane to the back of the RFIC.

Figures 6 and 7 illustrate the GND metal filled sections on the entire 4431-T-B1\_B test card PCB. The top and bottom layers are shown.

 


Figure 6. Ground Poured Sections with PCB Vias around the Matching Network (Top Layer)

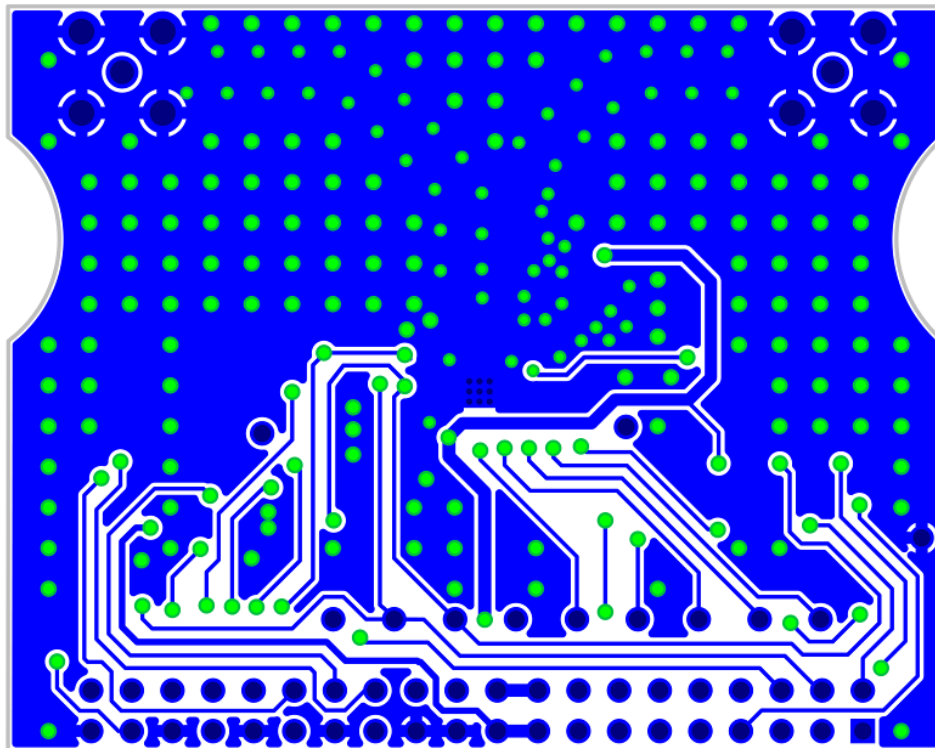


Figure 7. Ground Poured Sections with PCB Vias (Bottom Layer)

# AN414

- To reduce sensitivity to PCB thickness variation, use 50  $\Omega$  grounded coplanar lines wherever possible to connect the SMA connector(s) to the matching network and/or the RF switch. This also reduces radiation and coupling effects. The interconnections between the elements are not considered transmission lines because their lengths are much shorter than the wavelength and, thus, their impedance is not critical. As a result, their recommended width is the smallest possible (i.e. equal to the width of the pad of the applied components). In this way, the parasitic capacitances to ground can be minimized. In the case of the 4431-T-B1\_B type test card, the only routes where 50  $\Omega$  coplanar transmission line is used are between the output of the matching networks and the SMA connectors. Examples for the trace dimensions are shown in Table 1.

Figure 8 illustrates the 50  $\Omega$  grounded coplanar line of the TX side on the 4431-T-B1\_B test cards.

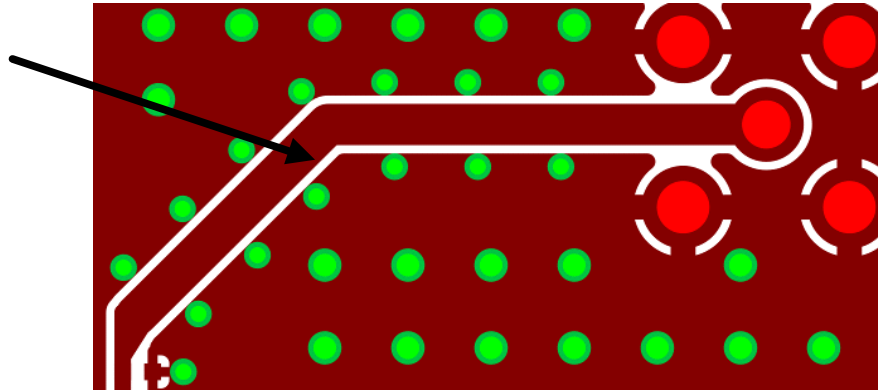


Figure 8. 50  $\Omega$  Grounded Coplanar Line on 1.5 mm Thick Substrate

Table 1. Parameters for 50  $\Omega$  Grounded Coplanar Lines

f	240–960 MHz	
T	0.018–0.035 mm	
Er	4.6	
H	1.5 mm	0.26 mm*
G	0.25 mm	0.64 mm
W	1.26 mm	0.45 mm

\*Note: For four-layer PCBs, the thickness between the top and the next inner layer should be taken into account.

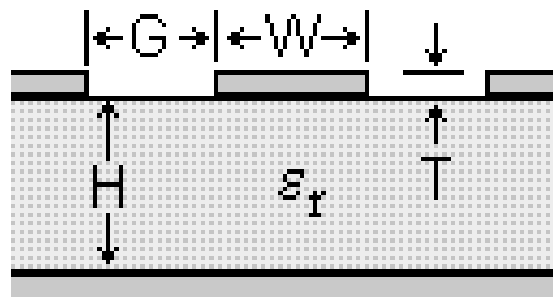


Figure 9. Grounded Coplanar Line Parameters



### 2.1.3. Direct Tie Type Matching Network Layout Based upon the 4431-T-B1\_D Test Card (Single Antenna without RF Switch)

For reference, layout examples shown in this section are based upon the layout of the 4431-T-B1\_D RF test cards. These boards contain a single antenna, and the TX and RX paths are connected directly together, without the use of an RF switch.

The schematic of the Direct Tie type matching network is shown in Figure 10. For this type of matching, an additional inductor is necessary at the RX side, forming a four-element RX matching network (described in “AN436: Si4030/4031/4430/4431 PA Matching”).

During TX mode operation, the built-in LNA protection circuit should be enabled by setting the `Ina_sw` bit of the TX Power register 6Dh to “1” (see “AN440: Si4430/31/32 Register Descriptions”). In this case, the dc path from the output of the matching network to GND is not blocked through the RX side; so, a dc blocking capacitor (CC1) is necessary.

In the case of Direct Tie type matching, coupling between the RX and TX sides is not critical since no harmonic leakage through the coupled RX path occurs; both of them are filtered after the common connection point.

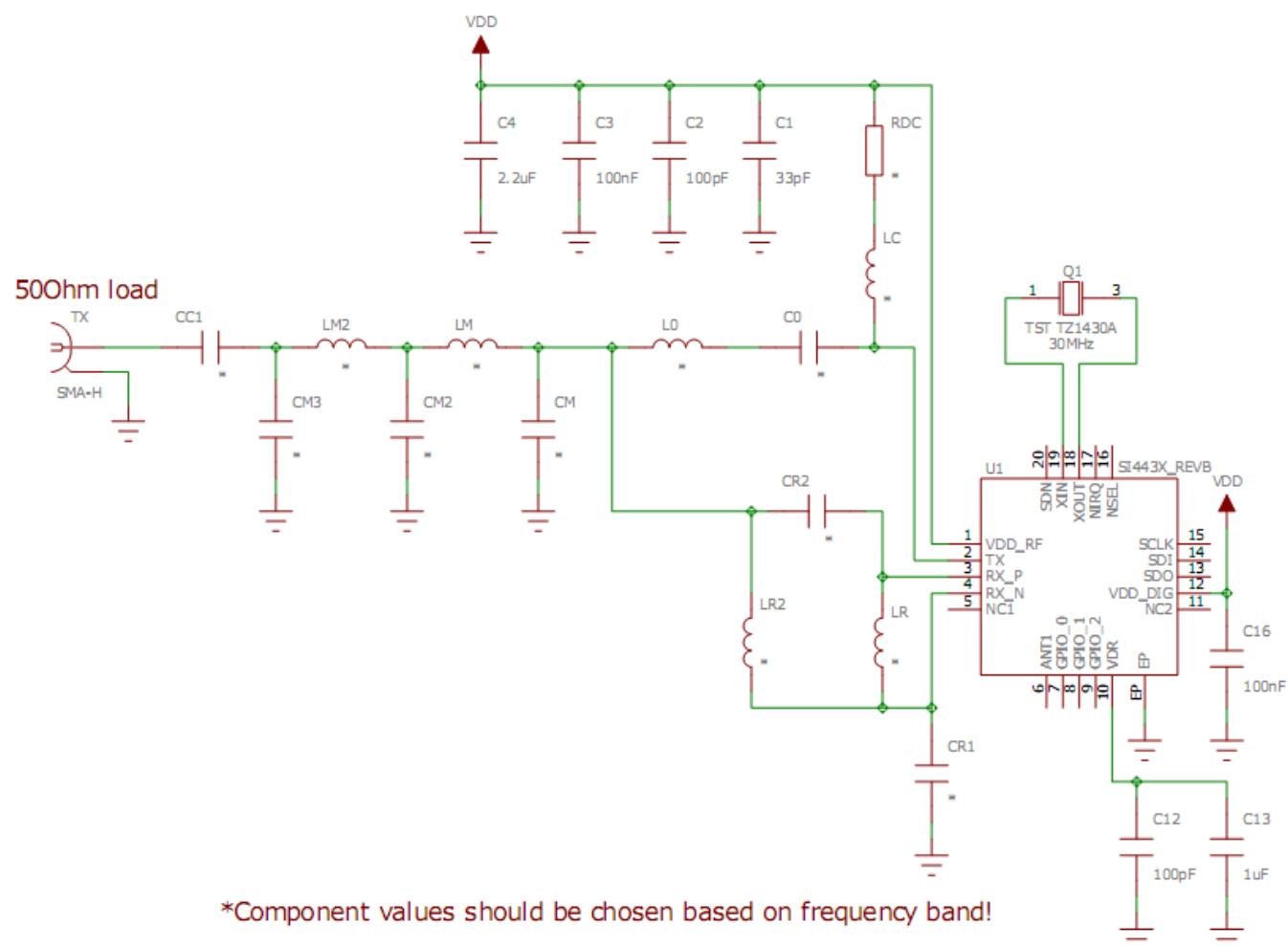


Figure 10. Schematic of the Direct Tie Type Matching Network

## 2.1.4. Layout Design Guidelines

The principles in this case are the same as for Split type matching, except for the following issues:

- To minimize the parasitics (i.e., the length) of the trace connecting the RX and TX sides, the RX side components are closer to the TX side components. Also, because of this, the nearby inductors are not perpendicular to each other.
- The trace parasitics are very critical for the connection of LR2; so, the shortest traces possible should be used for connecting LR2 to the TX side.
- Since the RX-TX coupling is not critical, there is not any separating GND metal between the two sides.

Figure 11 illustrates the positioning and orientation of components and ground pour flooding.

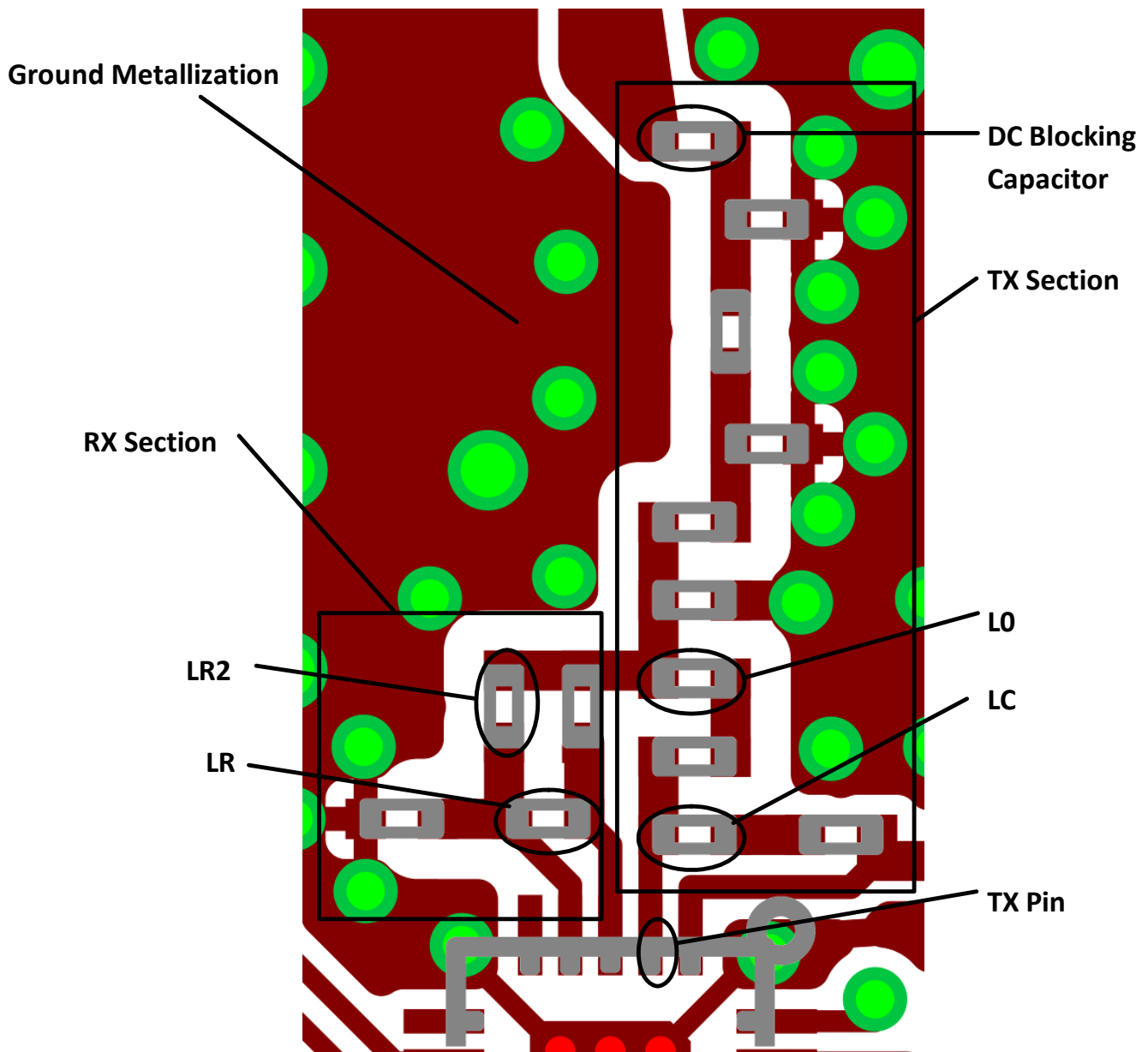


Figure 11. Direct Tie Matching Network Layout Structure

## 2.2. Guidelines for Layout Design when Using the Si4432

For the versions of RF test cards using the Si4432 RFIC (i.e., +20 dBm PA), similar general layout guidelines can be applied as described for the Si4431 RFIC (i.e., +13 dBm PA). However, some minimal additional filtering and circuitry must be implemented.

The increased TX output power of the Si4432 chip is accompanied by a corresponding increase in the absolute level of harmonic signals. Since most regulatory standards (e.g. FCC, ETSI, ARIB, etc.) require the harmonic signals to be attenuated below some absolute power level (in watts or dBm), the amount of low-pass filtering required is generally greater on an RF test card using an Si4432 chip. Thus, the RF test card layout for the Si4432 RFIC may contain a slightly higher number of components in the L-C lowpass filter.

Further, due to the increase in output power, it is necessary to pay closer attention to the shape and amplitude of the voltage waveform at the TX output pin of the device. Silicon Labs recommends that a harmonic termination circuit be placed in a parallel shunt-to-GND configuration at the input of the lowpass filter. This harmonic termination circuit helps maintain the desired voltage waveform at the TX output pin by providing a good impedance termination at very high harmonic frequencies. For further information on this subject, refer to “AN435: Si4032/4432 PA Matching”.

Unlike the Si4431, the test cards for the Si4432 are manufactured on a four-layer PCB. The purpose of this is to allow most traces to be placed on the inner layers while the outer layers function as shields for further reduction of the radiated levels of harmonics.

### 2.2.1. Switch Type Matching Network Layout Based upon the 4432-T-B1\_C Test Card (Single Antenna with RF Switch)

For reference, examples shown in this section are based upon the layout of the 4432-T-B1\_C RF test cards. These boards contain a single antenna and an RF switch to select between the TX and RX paths. The schematic of the Switch type matching network for the Si4432 RevB1 is shown in Figure 12.

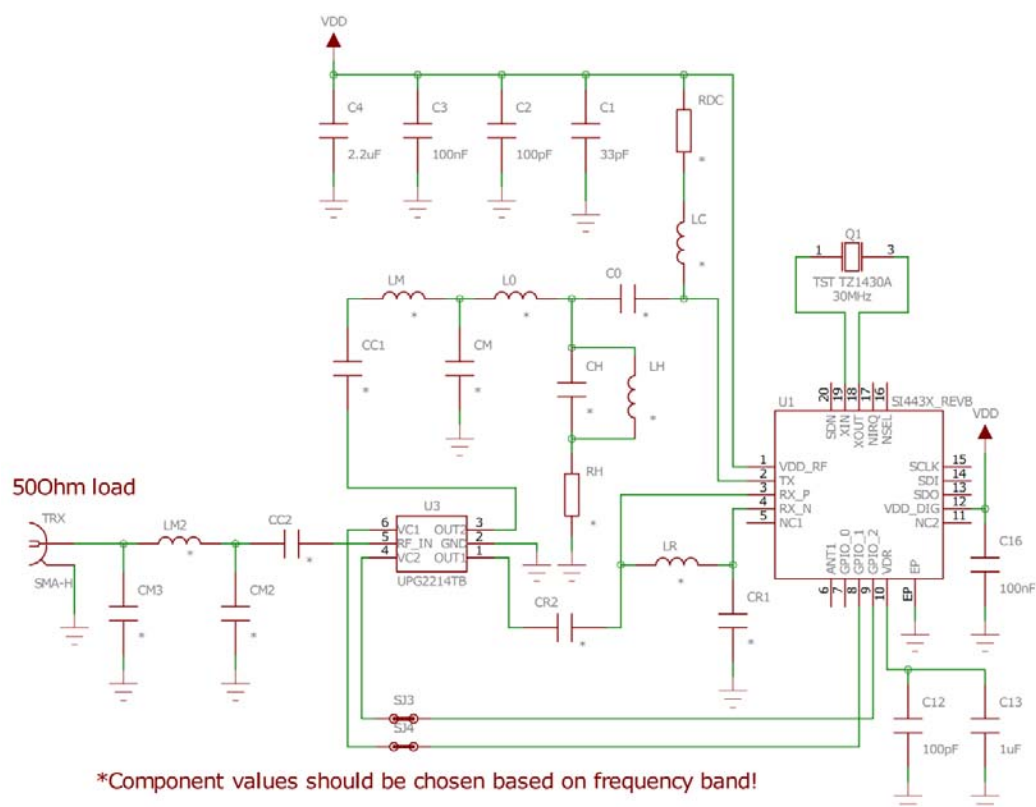


Figure 12. Schematic of the Switch Type Matching Network for the Si4432 Rev B1

## 2.2.2. Layout Design Guidelines

- When using a TX/RX switch, or a switch to select antennas in an antenna diversity implementation, a series capacitor may be required on all ports (e.g., TX, RX, Antenna) of the switch to block the dc patch between the switch and the ground. Refer to the exact requirements and specifications of the switch used in the application.
- RF switches may themselves behave in a slightly non-linear fashion, resulting in some re-generation of harmonic energy regardless of the cleanliness of the input signal to the switch. Thus it may be necessary to move a portion of the TX lowpass filter to after the RF switch (i.e., just prior to the antenna) in order to further attenuate these re-generated harmonic signals.
- If the RX side matching network is relatively far from the RF switch then the connecting trace should be a 50 $\Omega$  grounded coplanar line.
- The area between the RX and TX sides should be filled with GND metal to increase the isolation (just as in case of the Split type design).

Figure 13 demonstrates the positioning and orientation of components, ground flooding, and thermal strapping.


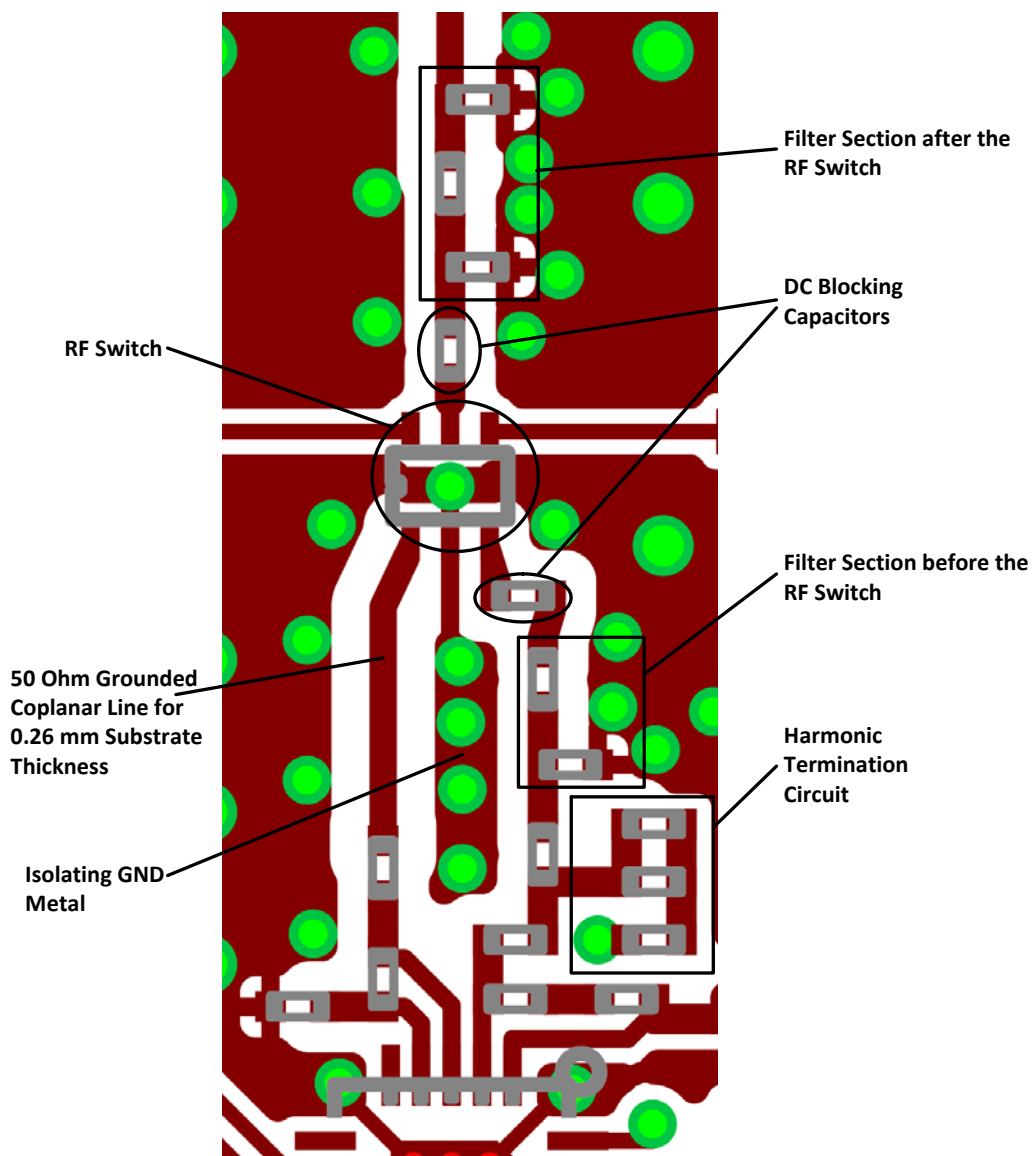


Figure 13. Si4432 Switch Type Matching, Component Orientation, Placement, and GND Metallization

The return path to GND of the harmonic termination circuit is important. This trace and current path should be kept as short as possible and should be allowed to return directly to the GND paddle of the RFIC; it should be connected to the GND metal only at that point. Also, to avoid coupling with the matching network itself, it should be routed on the second inner layer under the matching network, not on the first one (the first inner layer should be filled with ground metal under the matching network). Figure 14 demonstrates the dc return path of the harmonic termination circuit.

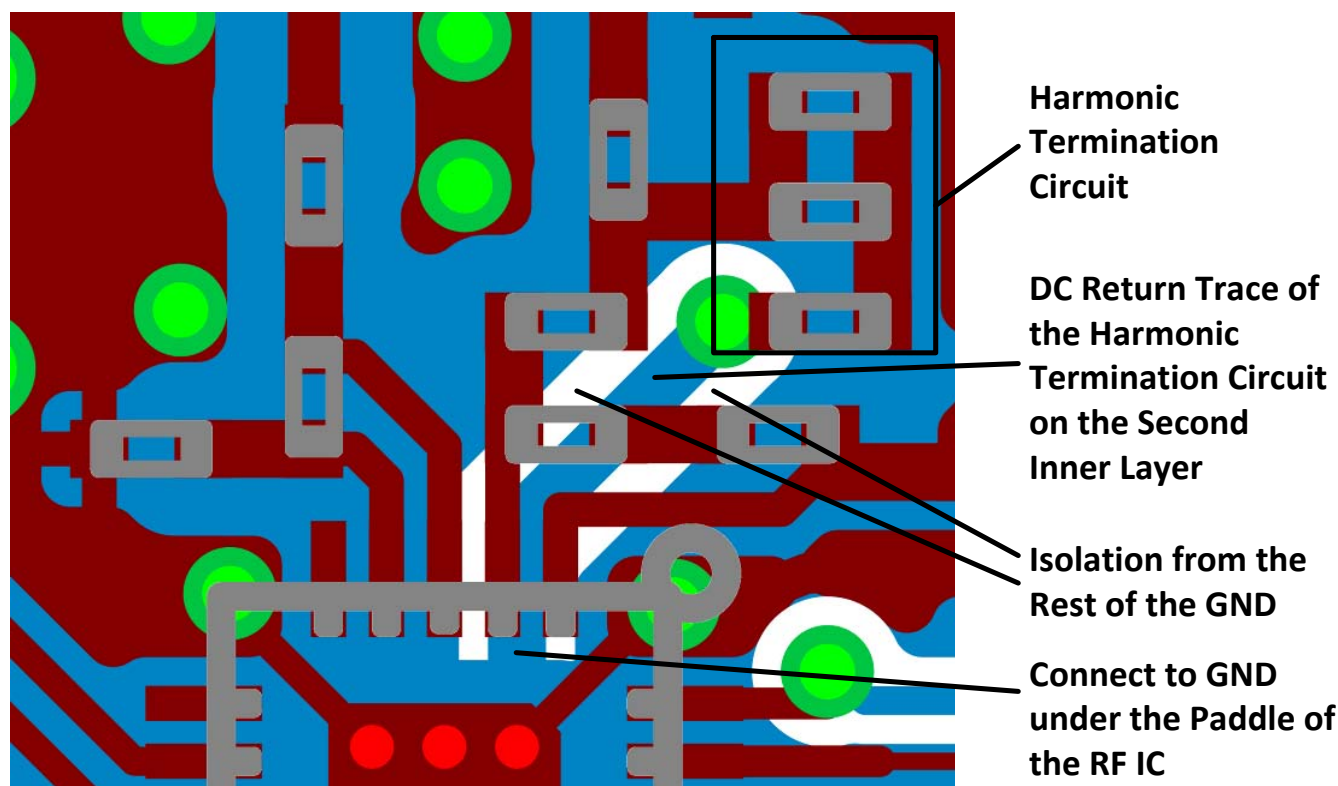

**Figure 14. DC Return Path on the Second Inner Layer  
(The First Inner Layer under the Top One is Suppressed)**

### 2.2.3. Diversity Type Matching Network Layout Based upon the 4432-T-B1\_A Test Card (Two Antennas with RF Switch)

The purpose of this type of test card is to demonstrate the Antenna Diversity feature of the EZRadioPRO RFICs. Antenna diversity is often used to provide better range in case of an obstructed environment where the range with a single antenna board configuration is lessened due to multipath fading and/or different RX antenna and TX field polarizations.

Multipath fading causes nulls in the radiated field of the TX with  $1/2$  wavelength period. To compensate for this, the separation distance of the antennas should be around  $1/4$  wavelength.

If the polarization of the radiated field is not parallel with the RX antenna, either because of the different polarization of the TX antenna or the polarization changes caused by reflections, then positioning the RX antennas perpendicular to the each other can help. (Refer to “AN379: Antenna Diversity with EZRadioPRO®” for further information on this subject.)

As with the Switch type matching network, a portion of the TX lowpass filter (LPF) should be placed after the RF switch to further attenuate any harmonics regenerated by the switch. Since, in this case, transmission is possible on both antennas, the portion of the LPF should be inserted into both paths.



### 3. Available Manufacturing Packs

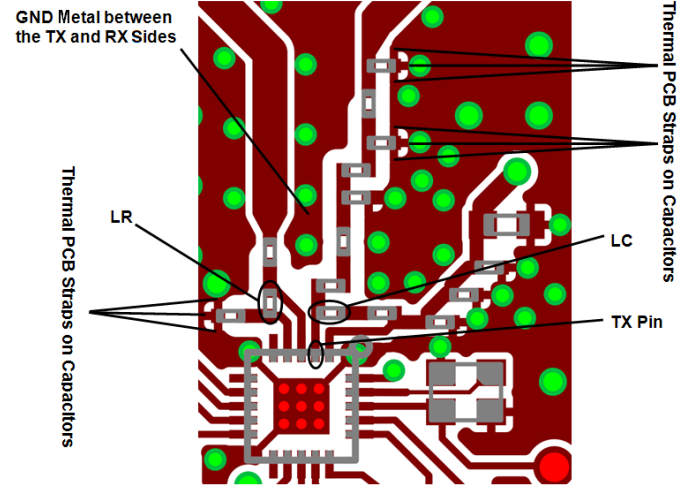
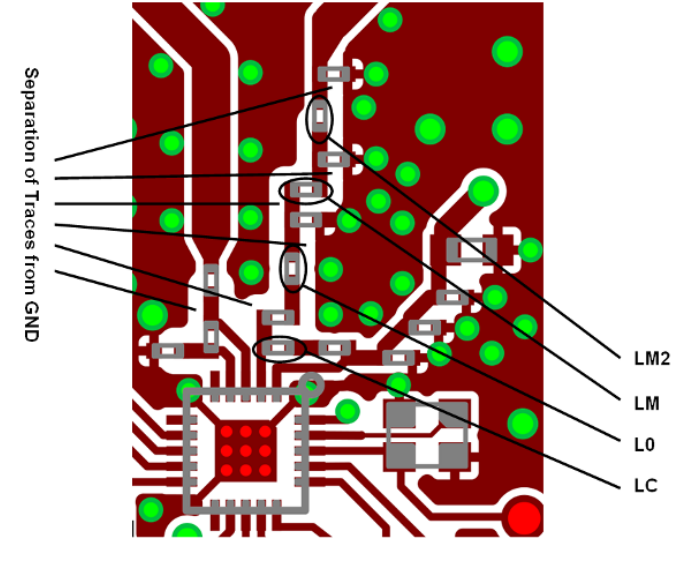
Table 2 contains a partial list of the reference design packs available for download on [www.silabs.com](http://www.silabs.com).

**Table 2. Available Manufacturing Packs**




Part Number	Frequency [MHz]	Antenna Configuration
4031-T-B1 B 434	434	Single antenna
4031-T-B1 B 868	868	Single antenna
4032-T-B1 B 470	470	Single antenna
4032-T-B1 B 915	915	Single antenna
4330-T-B1 B 434	434	Single antenna
4330-T-B1 B 470	470	Single antenna
4330-T-B1 B 868	868	Single antenna
4330-T-B1 B 915	915	Single antenna
4330-T-B1 B 950	950	Single antenna
4430-T-B1 B 950	950	Separate TX and RX designed for lab testing
4430-T-B1 D 950	950	Single antenna implemented without RF switch
4431-T-B1 B 434	434	Separate TX and RX designed for lab testing
4431-T-B1 D 434	434	Single antenna implemented without RF switch
4431-T-B1 B 868	868	Separate TX and RX designed for lab testing
4431-T-B1 D 868	868	Single antenna implemented without RF switch
4432-T-B1 B 470	470	Separate TX and RX designed for lab testing
4431-T-B1 C 470	470	Single antenna implemented with RF switch
4431-T-B1 D 470	470	Single antenna implemented without RF switch
4431-T-B1 B 915	915	Separate TX and RX designed for lab testing
4431-T-B1 C 915	915	Single antenna implemented with RF switch

## 4. Checklist


### 4.1. Main Layout Design Principles

1	Is the choke inductor (LC) as close to the TX pin as possible?	
2	Is the RX parallel inductor (LR) perpendicular to the choke inductor (LC) in the TX path? (except for the Direct Tie type matching)	
3	Is the TX and RX separated by a ground metal on the top layer? (except for the Direct Tie type matching)	
4	Are the neighboring matching network components as close to each other as possible?	
5	Are there more thermal straps used with the capacitors?	
6	Are the TX path inductors perpendicular to each other?	
7	Is there at least 0.5 mm separation in the matching between the traces/pads and the GND metal?	

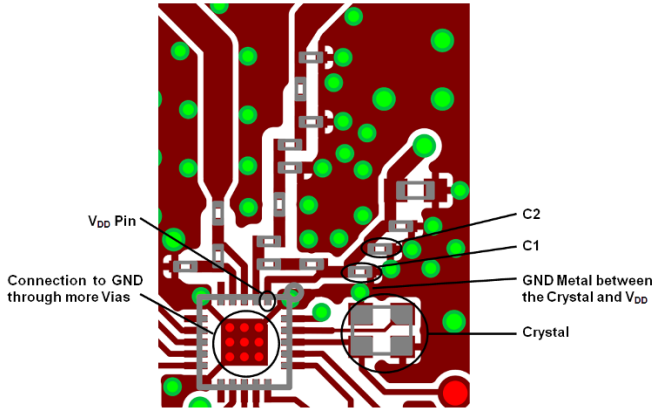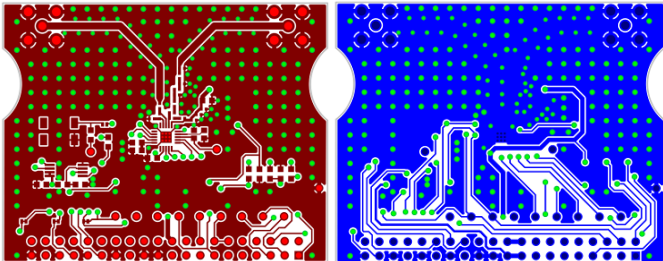
 


8	Are the smallest value VDD filter capacitors kept closer to the VDD pin of the RF IC?	
9	Does exposed pad footprint use more vias?	
10	Is the crystal as close to the RF IC as possible?	
11	Does ground metal exist between the crystal and the VDD feed?	
12	Was large, continuous GND metallization added to at least the RF sections?	
13	Was the area on the bottom layer under the matching network filled with GND metal and was wiring and routing avoided in this region?	
14	Were 50 Ω grounded coplanar lines used for connecting the matching network, the switch and/or the SMA connector(s)?	


## 4.2. Additional Concerns for Direct Tie Matching

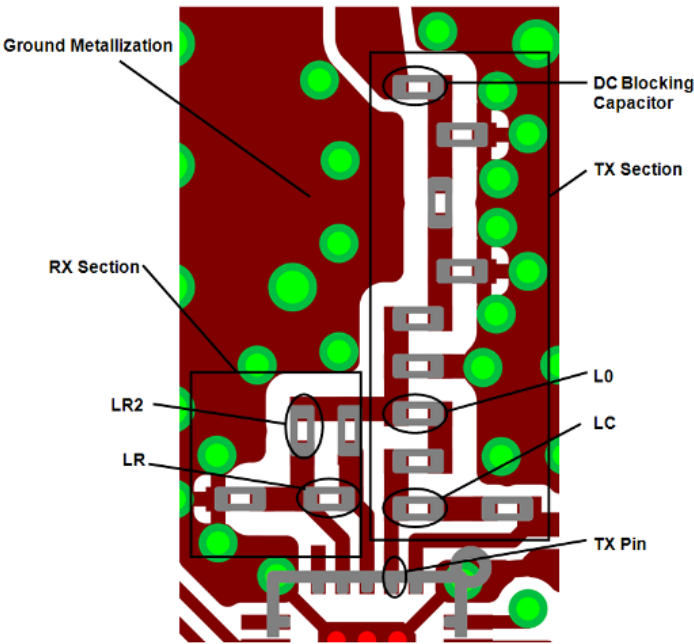15	Is the length of the trace connecting the RX and TX sides minimal?	 <p>The diagram shows a PCB layout with a central vertical trace. On the left side, there is an RX Section containing components LR, LR2, and L0. On the right side, there is a TX Section containing components L0, LC, and a TX Pin. A DC Blocking Capacitor is placed at the top of the central trace. The entire layout is surrounded by Ground Metallization, represented by green circles.</p>
16	Is LR2 connected with as short traces as possible?	
17	Is an additional dc blocking capacitor added to the output of the matching network to block the dc path in RX mode?	

4.3. Additional Concerns for the Si4432 and the Switch and Diversity Type Matching
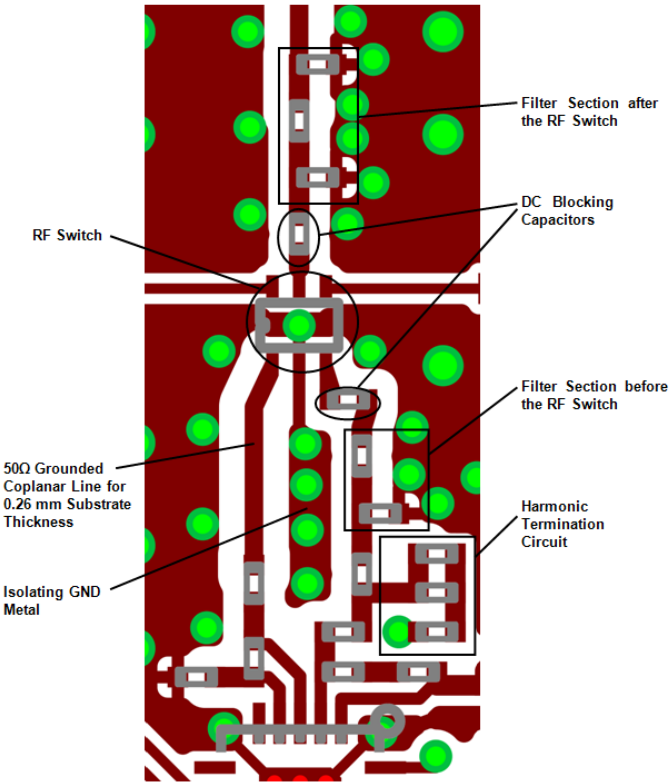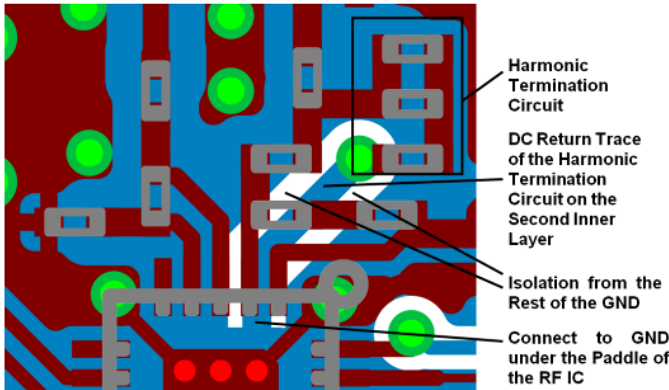
<p>18</p>	<p>Was the additional harmonic termination circuit added into the TX path?</p>	 <p>Filter Section after the RF Switch</p> <p>DC Blocking Capacitors</p> <p>Filter Section before the RF Switch</p> <p>Harmonic Termination Circuit</p> <p>RF Switch</p> <p>50Ω Grounded Coplanar Line for 0.26 mm Substrate Thickness</p> <p>Isolating GND Metal</p>
<p>19</p>	<p>Were series capacitors added to the TX path to block the dc when a TX/RX switch (or Diversity switch) is used?</p>	
<p>20</p>	<p>Was 50 Ω grounded coplanar line used for connecting the RX side matching to the RF switch (if they are far from each other)?</p>	
<p>21</p>	<p>Was the area between the RX and TX sides filled with GND metal?</p>	
<p>22</p>	<p>Was the dc return path of the harmonic termination circuit constructed properly?</p>	 <p>Harmonic Termination Circuit</p> <p>DC Return Trace of the Harmonic Termination Circuit on the Second Inner Layer</p> <p>Isolation from the Rest of the GND</p> <p>Connect to GND under the Paddle of the RF IC</p>

# AN414

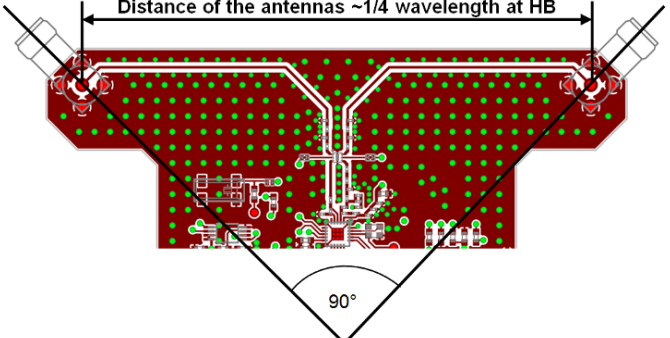23	Are the antennas perpendicular to each other?	
24	Is the distance of the antennas approximately 1/4 wavelength?	

## DOCUMENT CHANGE LIST

### Revision 0.1 to Revision 0.2

- Updated to latest reference designs



## Simplicity Studio

One-click access to MCU tools, documentation, software, source code libraries & more. Available for Windows, Mac and Linux!

[www.silabs.com/simplicity](http://www.silabs.com/simplicity)



**MCU Portfolio**  
[www.silabs.com/mcu](http://www.silabs.com/mcu)



**SW/HW**  
[www.silabs.com/simplicity](http://www.silabs.com/simplicity)



**Quality**  
[www.silabs.com/quality](http://www.silabs.com/quality)



**Support and Community**  
[community.silabs.com](http://community.silabs.com)

### Disclaimer

Silicon Laboratories intends to provide customers with the latest, accurate, and in-depth documentation of all peripherals and modules available for system and software implementers using or intending to use the Silicon Laboratories products. Characterization data, available modules and peripherals, memory sizes and memory addresses refer to each specific device, and "Typical" parameters provided can and do vary in different applications. Application examples described herein are for illustrative purposes only. Silicon Laboratories reserves the right to make changes without further notice and limitation to product information, specifications, and descriptions herein, and does not give warranties as to the accuracy or completeness of the included information. Silicon Laboratories shall have no liability for the consequences of use of the information supplied herein. This document does not imply or express copyright licenses granted hereunder to design or fabricate any integrated circuits. The products must not be used within any Life Support System without the specific written consent of Silicon Laboratories. A "Life Support System" is any product or system intended to support or sustain life and/or health, which, if it fails, can be reasonably expected to result in significant personal injury or death. Silicon Laboratories products are generally not intended for military applications. Silicon Laboratories products shall under no circumstances be used in weapons of mass destruction including (but not limited to) nuclear, biological or chemical weapons, or missiles capable of delivering such weapons.

### Trademark Information

Silicon Laboratories Inc., Silicon Laboratories, Silicon Labs, SiLabs and the Silicon Labs logo, CMEMS®, EFM, EFM32, EFR, Energy Micro, Energy Micro logo and combinations thereof, "the world's most energy friendly microcontrollers", Ember®, EZLink®, EZMac®, EZRadio®, EZRadioPRO®, DSPLL®, ISOmodem®, Precision32®, ProSLIC®, SiPHY®, USBXpress® and others are trademarks or registered trademarks of Silicon Laboratories Inc. ARM, CORTEX, Cortex-M3 and THUMB are trademarks or registered trademarks of ARM Holdings. Keil is a registered trademark of ARM Limited. All other products or brand names mentioned herein are trademarks of their respective holders.



**SILICON LABS**

Silicon Laboratories Inc.  
400 West Cesar Chavez  
Austin, TX 78701  
USA

<http://www.silabs.com>